

Homework #4 -

Problems 2.21 2.2<sup>2</sup> to 2.23 2.24 2.26 2.33 2.34

Engineering 378

Farnam Adelhani  
915815724

## 2.21

2.21 Draw the hardware obtained if the following code is synthesized:

```
module reg3 (Q1,Q2,Q3,Q4, A, CLK); %module name reg3
input A;
input CLK;
output Q1,Q2,Q3,Q4;
reg Q1,Q2,Q3,Q4;
always @(posedge CLK)
begin
Q4 = Q3;
Q3 = Q2;
Q2 = Q1;
Q1 = A;
end
endmodule
```

inputs: A, CLK

outputs: Q1, Q2, Q3, Q4

△ reg used for registers and counters, for data to be stored.

△ Q1, Q2, Q3, Q4 are on the hand side of = ...

they need to be stored till next assignment, so they are assigned to reg type.

△ Always @(posedge CLK): sequential statements executed when pos edge of clock occurs.

△ Blocking statements


Q4 = Q3;

Q3 = Q2; ⇒ only @ pos edge clk

Q2 = Q1;

Q1 = A;

4-Bit shift register

 


2.22 Draw the hardware obtained if the following code is synthesized:

```
module reg3 (Q1,Q2,Q3,Q4, A,CLK);
input A;
input CLK;
output Q1,Q2,Q3,Q4;
reg Q1,Q2,Q3,Q4;
always @(posedge CLK)
begin
```

```
Q1 = A;
Q2 = Q1;
Q3 = Q2;
Q4 = Q3;
end
endmodule
```

Blocking  
statements

 


2.23 Draw the hardware obtained if the following two modules are synthesized and describe the differences.

```
module reg3 (Q1,Q2,Q3,Q4,A,CLK);
input A;
input CLK;
output Q1,Q2,Q3,Q4;
reg Q1,Q2,Q3,Q4;
// first
always @(posedge CLK)
begin
Q1 <= A;
Q2 <= Q1;
Q3 <= Q2;
Q4 <= Q3;
end
endmodule
```

```
module reg3 (Q1,Q2,Q3,Q4,A,CLK);
input A;
input CLK;
output Q1,Q2,Q3,Q4;
reg Q1,Q2,Q3,Q4;
// first -> second
always @(posedge CLK)
begin
Q4 <= Q3;
Q3 <= Q2;
Q2 <= Q1;
Q1 <= A;
end
endmodule
```

The sequential statements  
can be evaluated in any  
order, so the two  
modules are similar/identical

4-bit shift register

 

- 2.24 (a) Assume  $D_1=0$ ,  $D_2=5$ , and  $D_1$  changes to 1 at time=10ns. What are the values of  $D_1$  and  $D_2$  after the following code has been executed once? Do the values of  $D_1$  and  $D_2$  swap?

```
always @ (D1)
begin
    D2 <= D1;
    D1 <= D2;
end
```

Non-Blocking - simultaneous execution

- (b) Assume  $D_1=0$ ,  $D_2=5$ , and  $D_1$  changes to 1 at time=10ns. What are the values of  $D_1$  and  $D_2$  after the following code has been executed once? Do the values of  $D_1$  and  $D_2$  swap?

```
always @ (D1)
begin
    D2 = D1;
    D1 = D2;
end
```

Blocking - sequential

- (c) How many latches will result when the following code is synthesized? Assume B is 3 bits long.

```
always @ (State) begin
    case(State)
        2'b00: B = 5;
        2'b01: B = 3;
        2'b10: B = 0;
        2'b11: B = 0;
    endcase
end
```

2'b11 not included

Circle the correct choice:

- 1 latch because 1 case is missing
- 2 latches because state is 2 bits
- 3 latches because B is 3 bits
- 5 latches because B is 3 bits and state is 2 bits
- None of the above. But it results in \_\_\_\_\_ latches.

(a)  $D_1 = 0 \Rightarrow D_1 = 5 = 1$   
 $D_2 = 5 \Rightarrow D_2 = 1 = 5$

Values of  $D_1$  &  $D_2$  swap

(b) The statement is Blocking and thus, sequential.

(c) output is 3-bit wide (0-000, 5-101, 3-011)  
 8 latches

- 2.26 For the following Verilog code, assume that D changes to 1 at time 5ns. Give the values of A, B, C, D, E, and F each time a change occurs. That is, give the values at time 5ns, 5 +  $\Delta$ , 5 + 2 $\Delta$ , and so forth. Carry this out until 20 steps have occurred, until no further change occurs, or until a repetitive pattern emerges.

```
module prob(D);
inout D;
wire A, C;
reg B, E, F, temp_D;

initial
begin
    B = 1'b0;
    E = 1'b0;
    F = 1'b0;
    temp_D = 1'b0;
end

assign C = A;
assign A = (B & !E) | D;
assign D = temp_D;

always @(A)
begin
    B = A;
end

always
begin
    wait(A)
    E <= #5 B;
    temp_D <= 1'b0;
    F <= E;
end
endmodule
```

ns + A	A	B	C	D	E	F
0 0	0	0	0	0	0	0
5 0	0	0	0	1	0	0
5 1	1	0	0	1	0	0
5 2	1	1	1	1	0	0
6 0	1	1	1	0	0	0
10 0	1	1	1	0	1	0
10 1	0	1	1	0	1	1
10 2	0	0	0	0	1	1
11 0	0	0	0	0	1	1
15 0	0	0	0	0	0	1
15 1	0	0	0	0	0	0

2.33 If  $A = 101$ ,  $B = 011$ , and  $C = 010$ , what are the values of the following statements?  
Assume A, B, and C are of reg type. Assume as many bits as necessary for the result.

- (a)  $\{A, B\} \mid \{B, C\}$   
(b)  $A \gg 2$

- (c)  $A \ggg 2$   
(d)  $\{A, (\sim B)\} == 111110$   
(e)  $A \mid B \& C$

Ⓐ concatenation  $\{A, B\} = 101011$   $\{B, C\} = 011010$   
OR operator is performed

111011

Ⓑ  $A \gg 2 \rightarrow$  001

Ⓒ  $A \ggg 2 \rightarrow$  111

Ⓓ  $\{A, (\sim B)\} == 111110$

$(\sim B) = 100 \dots \{A, (\sim B)\} = 101100 \neq 111110$

Not equal so result is 0

Ⓔ  $A \mid B \& C$

$B \& C = (011) \& (010) = 010$

$A \mid B \& C = 101 \mid 010 =$  111

2.34 Consider the following Verilog code:

```

module Q3(A,B,C,F,Clk,E);
input  A,B,C,F,Clk;
output reg E;

reg D,G;


initial
begin
    E = 1'b0;
    D = 1'b0;
    G = 1'b0;
end

always @(posedge Clk)
begin
    D <= A & B & C;
    G <= ~A & ~B;
    E <= D | G | F;
end

endmodule

```

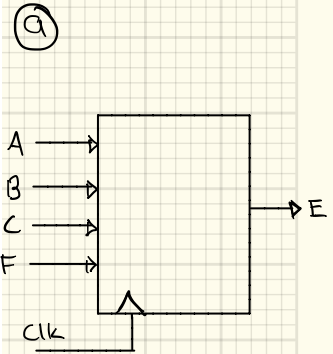- (a) Draw a block diagram for the circuit (no gates and at block level only).  
 (b) Give the circuit generated by the preceding code (at the gate level).



②

