

Engr 378 HW #5      2.36, 2.37, 2.43, 2.44, 2.48, 2.50

Engineering 378

Farnam Adelhkhani  
915815724


2.36 Draw the circuit represented by the following Verilog process:

```

always @(clk,clr)
begin
    if(clr == 1'b1)
        Q <= 1'b0;
    else if(clk == 1'b0 && CE == 1'b1)
        begin
            if(C == 1'b0)
                Q <= A & B;
            else
                Q <= A | B;
        end
    end
end

```

 
Why is *clr* on the sensitivity list whereas *C* is not?



2.37 (a) Write a conditional signal assignment statement to represent the 4-to-1 MUX shown subsequently. Assume that there is an inherent delay in the MUX that causes the change in output to occur 10ns after a change in input.

(b) Repeat (a) using an if-else statement.

(c) Repeat (a) using a case statement.

 

Ⓐ Conditional Statement for 4 to 1 MUX w/ delay 10 ns.

assign #10 F = (C == 0) ? (C == 0) ? ~A : B : (C == 0) ? ~B : 0;

Ⓑ always @(\*)

begin

if (C == 0 && D == 0)

#10 F = ~A;

else if (C == 0 && D == 1)

#10 F = B;

else if (C == 1 && D == 0)

#10 F = ~B;

else

#10 F = 0;

end

© 4-to-1 MUX w/ inherent delay of 10ns

always @ (\*)

begin

case (sel)

0: #10 F = ~A;

1: #10 F = B;

2: #10 F = ~B;

3: #10 F = 0;

end case

end

2.43 Write a Verilog module that describes a 16-bit serial-in, serial-out shift register with inputs *SI* (serial input), *EN* (enable), *CK* (clock, shifts on rising edge), and a serial output (*SO*).

Module ShiftReg (SI, EN, CK, SO);

input SI, EN, CK

output SO;

output [15:0] F;

reg [15:0] R;

initial begin

R <= 0

end

always @ (posedge CK)

begin if (EN == 1)

R <= {SI, register [15:1]};

end

assign SO = register [0];


assign F = register;

end module

 2.44 A description of a 74194 4-bit bidirectional shift register follows.

The  $CLRB$  input is asynchronous and active low and overrides all the other control inputs. All other state changes occur following the rising edge of the clock. If the control inputs  $S_1 = S_0 = 1$ , the register is loaded in parallel. If  $S_1 = 1$  and  $S_0 = 0$ ,

the register is shifted right and  $SDR$  (serial data right) is shifted into  $Q_3$ . If  $S_1 = 0$  and  $S_0 = 1$ , the register is shifted left and  $SDL$  is shifted into  $Q_0$ . If  $S_1 = S_0 = 0$ , no action occurs.



- (a) Write a behavioral-level Verilog model for the 74194.
- (b) Draw a block diagram and write a Verilog description of an 8-bit bidirectional shift register that uses two 74194s as components. The parallel inputs and outputs to the 8-bit register should be  $X([7:0])$  and  $Y([7:0])$ . The serial inputs should be  $RSD$  and  $LSD$ .


```

① module biShiftReg74194 (D, S1, SDR, SDL, CLRB, CLK, Q);
    input [3:0] D;
    input [1:0] S;
    input SDR, SDL, CLRB, CLK;
    output reg [3:0] Q;
    initial begin
        Q <= 0;
    end
    always @(CLK, CLRB)
        begin
            if (CLRB == 0)
                Q <= 4'b0000;
            else if (CLK == 1)
                begin
                    case (S)
                        0: Q <= Q;
                        1: Q <= {Q[2:0], SDR};
                        2: Q <= {SDR, Q[3:1]};
                        3: Q <= 0;
                    endcase
                end
        end
end module

```

(a) Write a behavioral level Verilog model for the 74194.

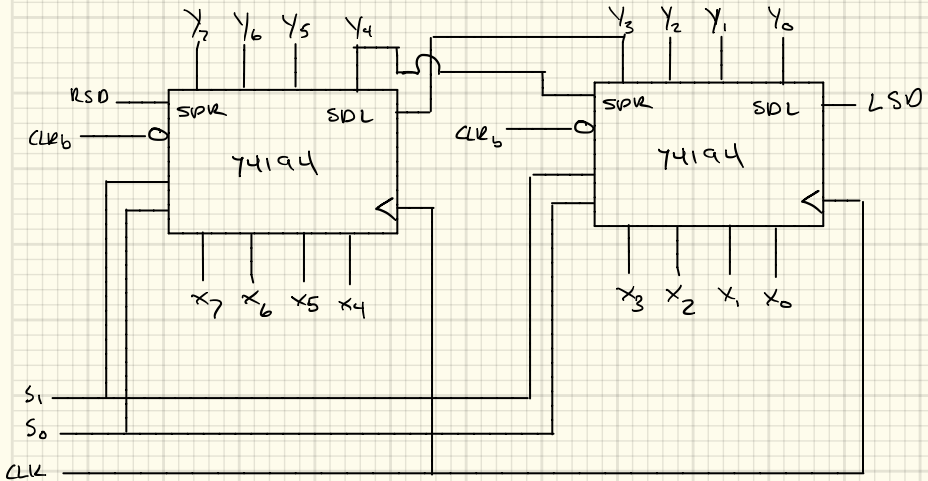(b) Draw a block diagram and write a Verilog description of an 8-bit bidirectional shift register that uses two 74194s as components. The parallel inputs and outputs to the 8-bit register should be  $X[7:0]$  and  $Y[7:0]$ . The serial inputs should be  $RSD$  and  $LSD$ .



```

module biShiftReg 8bit (X, S, RSD, LSD, CLRb, CLK, Y);
    input [7:0] X;
    input [1:0] S;
    input RSD, LSD, CLRb, CLK;
    output [7:0] Y;
    biShiftRegister 74194 S1(X[3:0], S, Y[4], LSD, CLRb, CLK,
        Y[3:0];
    biShiftRegister 74194 S2(X[7:4], S, RSD, Y[3], CLRb, CLK,
        Y[7:4];
end module
    
```

2.48 Complete the following Verilog code to implement a counter that counts in the following sequence:  $Q = 1000, 0111, 0110, 0101, 0100, 0011, 1000, 0111, 0110, 0101, 0100, 0011, \dots$  (repeats). The counter is synchronously loaded with 1000 when  $Ld8 = 1$ . It goes through the prescribed sequence when  $Enable = 1$ . The counter outputs  $S_5 = 1$  whenever it is in state 0101. Do not change the provided structure of the following module in any way. Your code must be synthesizable.

```
module countQ1(clk,Ld8,Enable,S5,Q);
input clk,Ld8,Enable;
output reg S5;
output reg[3:0] Q;
.
.
.
endmodule
```

```
module countQ1 (clk, Ld8, Enable, S5, Q);
    input clk, Ld8, Enable;
    output S5;
    output [3:0] Q;
    reg [3:0] Qtemp;
    initial begin
        Qtemp = 0;
    end
    always @ (pos edge clk)
        begin
            if (Ld8 == 1)
                Qtemp <= 4'b1000;
            else if (Enable == 1)
                begin
                    if (Qtemp == 4'b1000)
                        Qtemp <= 4'b1000;
                    else
                        Qtemp <= Qtemp - 1;
                end
            assign S5 = (Qtemp == 4'b0101) ? 1 : 0;
            assign Q = Qtemp;
        end
endmodule
```

2.50 Examine the following Verilog code and answer the following questions

```

module Problem(X,CLK,Z1,Z2);
input X,CLK;
output Z1,Z2;
reg [1:0]State,Nextstate;
initial
begin
    State = 2'b00;
    Nextstate = 2'b00;
end
always @(State,X)
begin
    case(State)
    0:begin
        if(X == 1'b0)begin
            Z1 = 1'b1;
            Z2 = 1'b0;
            Nextstate = 2'b00;
        end
        else begin
            Z1 = 1'b0;
            Z2 = 1'b0;
            Nextstate = 2'b01;
        end
    end
    1:begin
        if(X == 1'b0)begin
            Z1 = 1'b0;
            Z2 = 1'b1;
            Nextstate = 2'b01;
        end
        else begin
            Z1 = 1'b0;
            Z2 = 1'b1;
            Nextstate = 2'b10;
        end
    end
    2:begin
        if(X == 1'b0)begin
            Z1 = 1'b0;
            Z2 = 1'b1;
            Nextstate = 2'b10;
        end
        else begin
            Z1 = 1'b0;
            Z2 = 1'b1;
            Nextstate = 2'b11;
        end
    end
    3:begin
        if(X == 1'b0)begin
            Z1 = 1'b0;
            Z2 = 1'b0;
            Nextstate = 2'b00;
        end
        else begin
            Z1 = 1'b1;
            Z2 = 1'b0;
            Nextstate = 2'b01;
        end
    end
    endcase
end
always @(posedge CLK)
begin
    State <= Nextstate;
end
endmodule

```

(a)



(b)

| current<br>state | Next<br>state | X=0 | X=1 |    |    |    |
|------------------|---------------|-----|-----|----|----|----|
|                  | X=0           | X=1 | Z1  | Z2 | Z1 | Z2 |
| S0               | S0            | S1  | 1   | 0  | 0  | 1  |
| S1               | S1            | S2  | 0   | 1  | 0  | 1  |
| S2               | S2            | S3  | 0   | 1  | 0  | 1  |
| S3               | S0            | S1  | 0   | 0  | 1  | 0  |

- (a) Draw a block diagram of the circuit implemented by this code.  
 (b) Write the state table that is implemented by this code.