

Homework #7 3.14 -- 3.15 -- 3.16

Engineering 378


Farnam Adelkhani
915815724

3.14 (a) Implement the function $F_1 = A'BC + B'C + ABC$ using an FPGA with programmable logic blocks consisting of 4-to-1 multiplexers. Assume inputs and their complements are available as shown in Figure 3-34.

(b) Implement the function $F_1 = A'B + AB' + AC' + A'C$ using a multiplexer. What is the size of the smallest multiplexer needed, assuming inputs and their complements are available?


(A) $F_1 = \bar{A}BC + \bar{B}C + ABC$ can be implemented w/ an FPGA w/ prog. logic blocks

inputs			outputs	Mux input in terms of $\{0, 1, C, \bar{C}\}$
A	B	C	F_1	
0	0	0	0	C
0	0	1	1	
0	1	0	0	C
0	1	1	1	
1	0	0	0	C
1	0	1	1	
1	1	0	1	1
1	1	1	1	

 


(B)


inputs			outputs	Mux input in terms of $\{0, 1, C, \bar{C}\}$
A	B	C	F_1	
0	0	0	0	C
0	0	1	1	
0	1	0	0	1
0	1	1	1	
1	0	0	0	1
1	0	1	1	
1	1	0	1	\bar{C}
1	1	1	1	

 

 - 3.15 a) Route the "w", "x", "y", and "z" nets on the non-segmented tracks shown in the diagram that follows. Use the minimum number of tracks possible.
- b) Route the "w", "x", "y", and "z" nets on the segmented tracks shown in the diagram that follows. Use the minimum number of tracks possible.



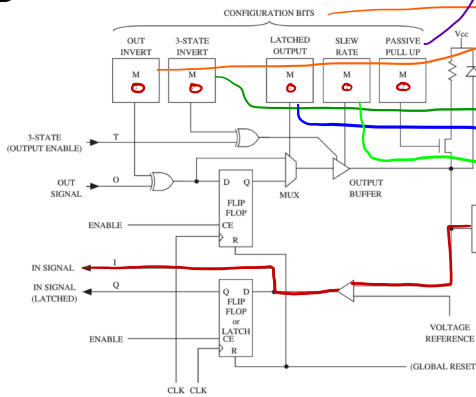- 3.16 Consider the following programmable I/O block:



Highlight the connections to configure this I/O block as an INPUT pin. Specify the five configuration bits.

- avoid floating points of output signal.
- allow control of aspects of I/O blocks
- 1 - inverts output using exclusive OR
- 0 - acts as a buffer
- when block acts as input so assuming it is 0
- generate active high/low state control signal
- when I/O block is used as input the output buffer must be in high-impedance state and hence the configuration bit is 0
- provide output in latched or complemented form
- ... since not using I/O block this is 0
- controls rate at which output signal can be changed
- ... since not using I/O block this is 0.